

FZU ID : 831903230

MU ID : 19104294

CS220 Computer Architecture

NAME : MENGYU RAO

Digital Logic Design

Practical 3

Part A

(a) Plot the function $f(A,B,C,D) = \sum m(0,4,5,8,9,10,12)$ on a k-map. You may need to draw a truth table first.

Truth table:

A	B	C	D	f
0	0	0	0	1
0	0	1	0	0
0	0	0	1	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

k-map:


AB \ CD	00	01	11	10
00	1	1	1	1
01	0	1	0	1
11	0	0	0	0
10	0	0	0	1

(b) Using the minimisation procedure on the k-map, write a minimal Sum-of-Products expression for the function f using AND, OR and NOT operators.


$$\begin{aligned}f &= \overline{C}\overline{D} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}B\overline{D} \\&= \overline{C}\overline{D} + \overline{C}(\overline{A}\overline{B} + \overline{A}B) + \overline{A}B\overline{D}\end{aligned}$$

(c) Implement the function on the simulator and verify its behaviour against the K-map (or truth table) for the function.


A=0 B=0 C=0 D=0 f=1

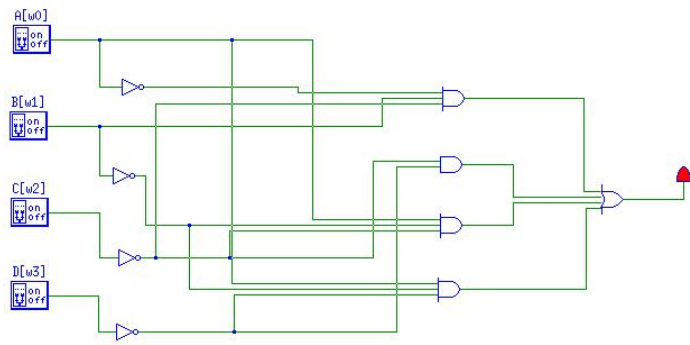


A=0 B=0 C=0 D=1 f=0

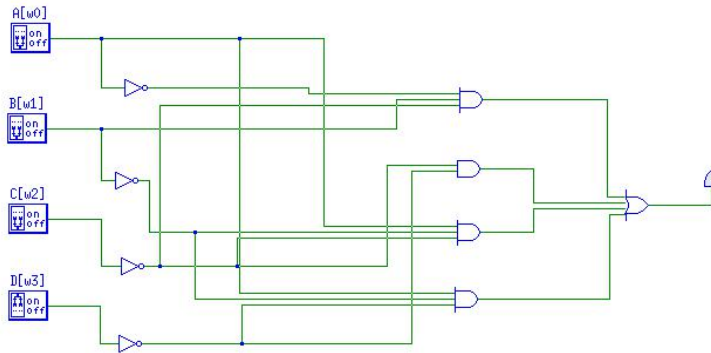


A=0 B=0 C=1 D=0 f=0

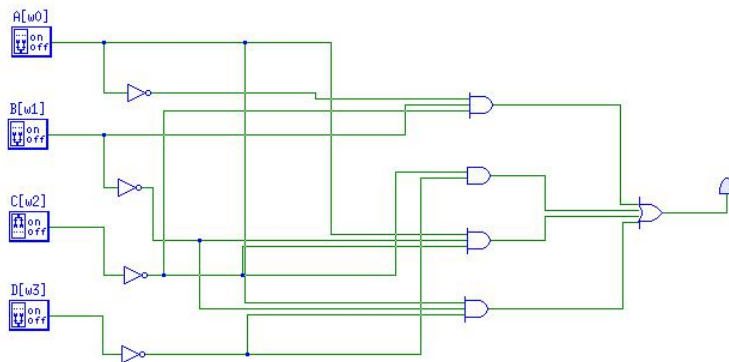


A=0 B=0 C=1 D=1 f=0

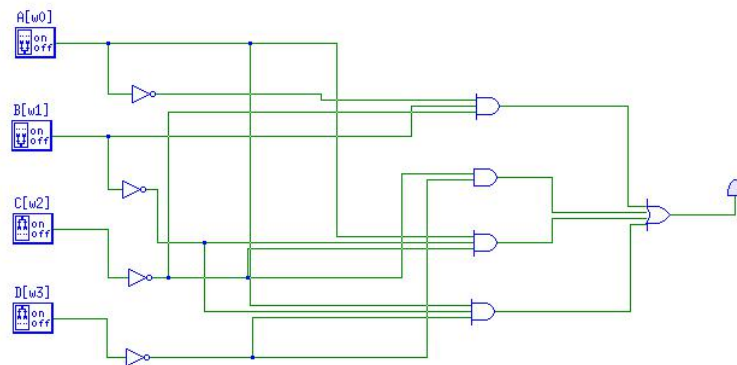


A=0 B=1 C=0 D=0 f=1

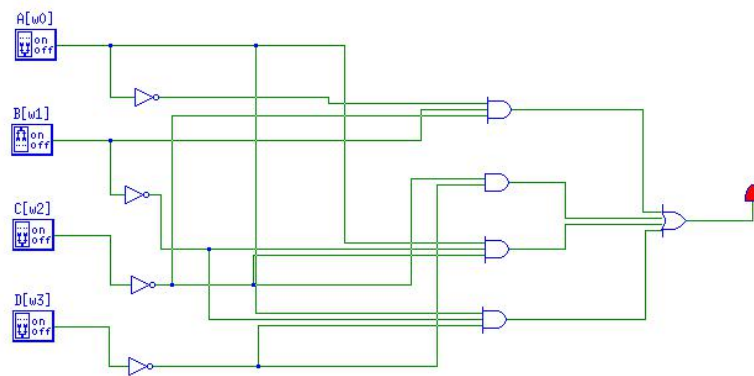


A=0 B=1 C=0 D=1 f=1

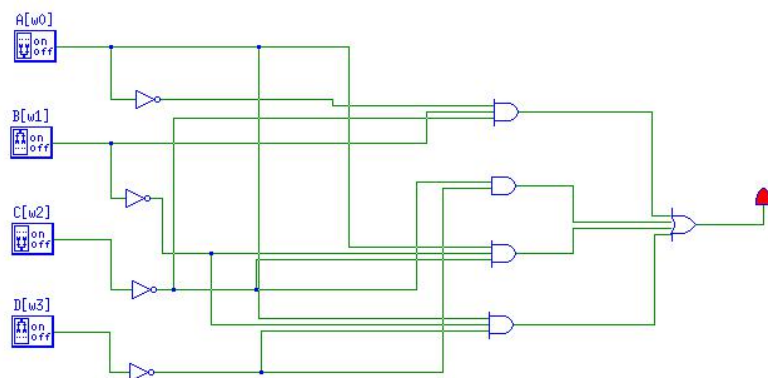


A=0 B=1 C=1 D=0 f=0

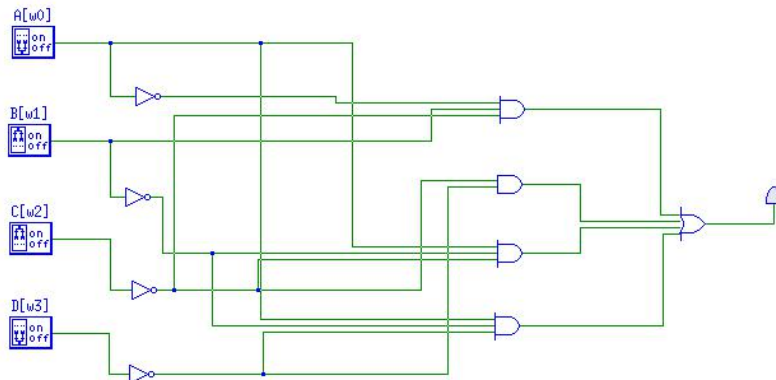


A=0 B=1 C=1 D=1 f=0

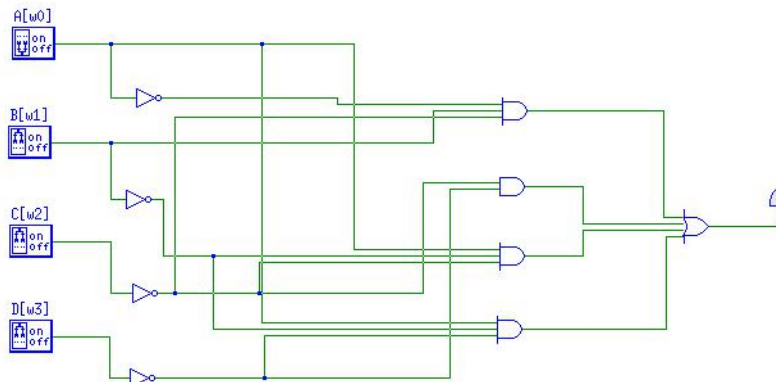


A = 1 B = 0 C = 0 D = 0 f = 1

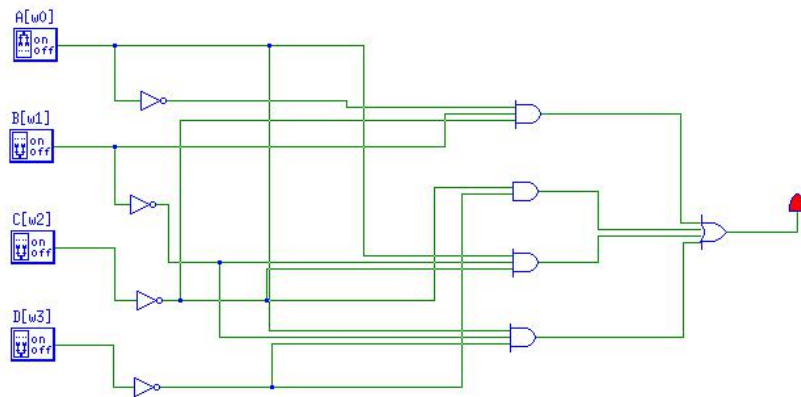


A = 1 B = 0 C = 0 D = 1 f = 1

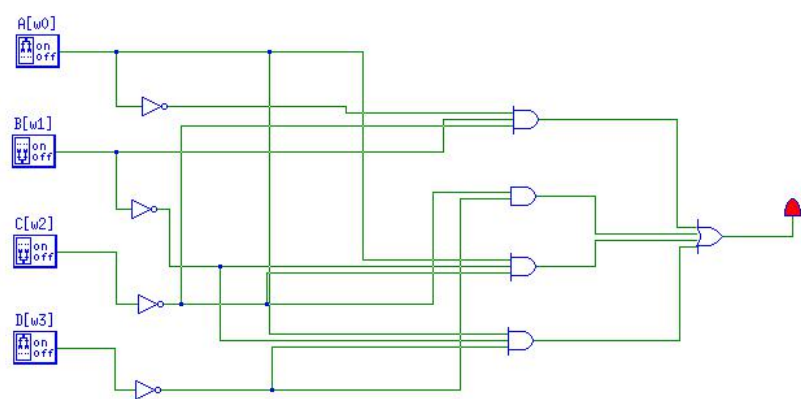


A = 1 B = 0 C = 1 D = 0 f = 1

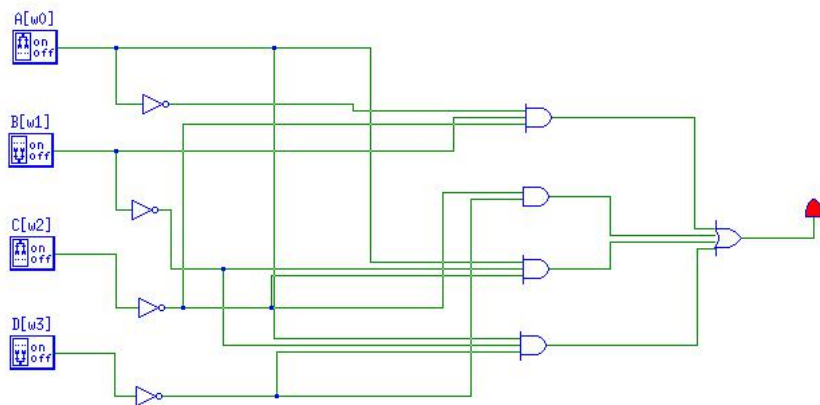


A = 1 B = 0 C = 1 D = 1 f = 0

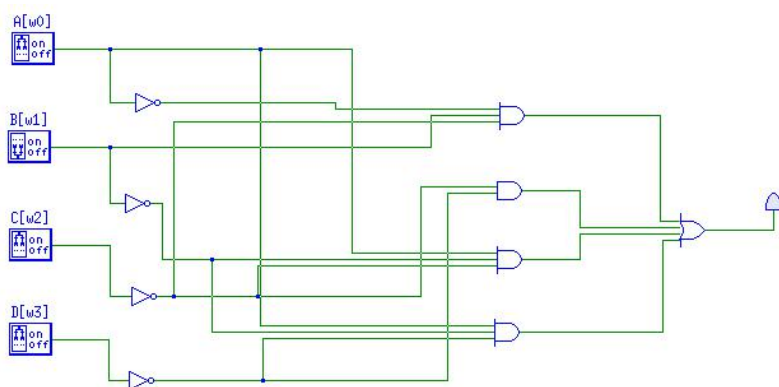


A = 1 B = 1 C = 0 D = 0 f = 1

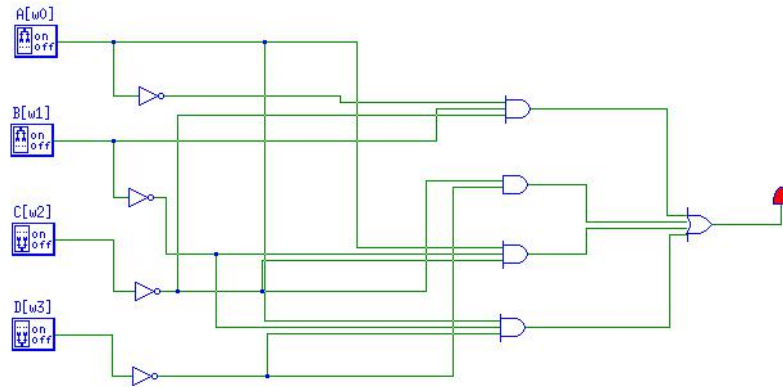


A = 1 B = 1 C = 0 D = 1 f = 0

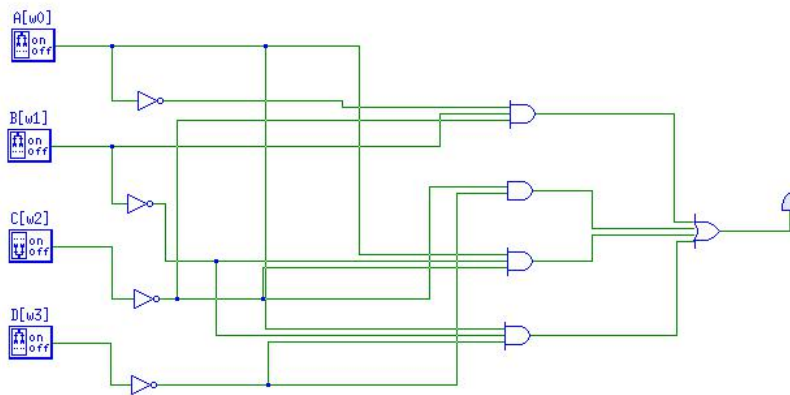

A = 1 B = 1 C = 1 D = 0 f = 0

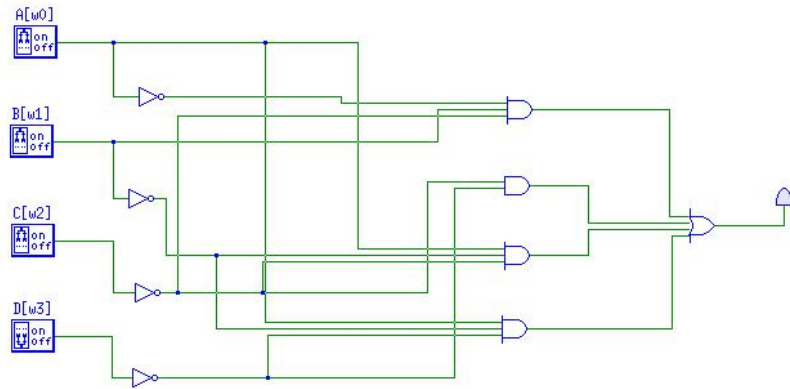


A = 1 B = 1 C = 1 D = 1 f = 0

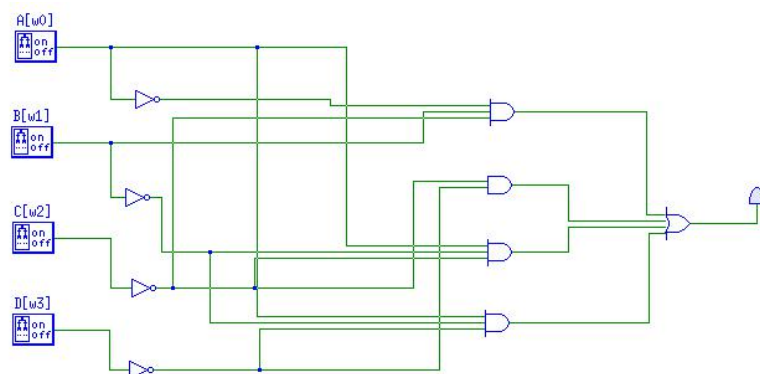

Part B

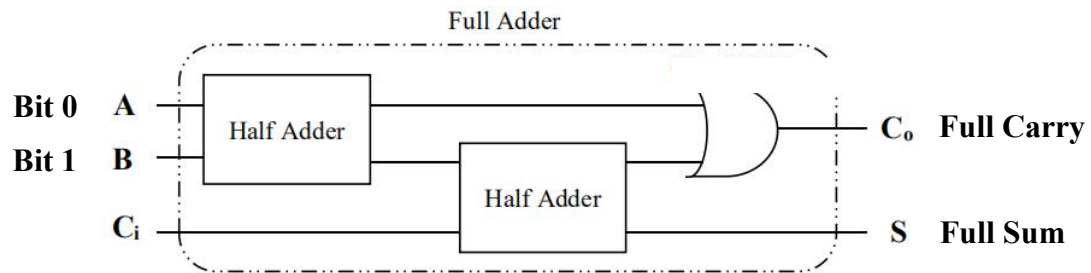(a) Draw a truth table for a 1-bit full adder circuit.



A	B	C_i	S	C_o
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

(b) Plot the sum and carry functions on separate k-maps.

Sum function on k-map:

AB \ C	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$S = A \oplus B \oplus C_i$$


Carry function on k-map:

AB \ C	00	01	11	10
0	0	0	1	0
1	0	1	1	1


$$C_o = AB + (A \oplus B)C_i$$

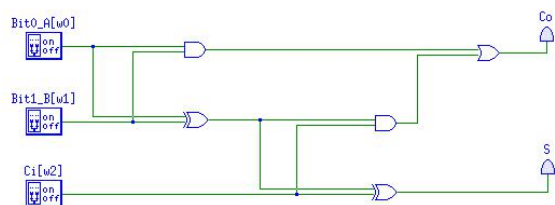(c) Design and construct a 1-bit full adder using only five two-input logic gates (either EXOR, OR, AND, NOT)


$A = 0 \quad B = 0 \quad C_i = 0 \quad S = 0 \quad C_o = 0$



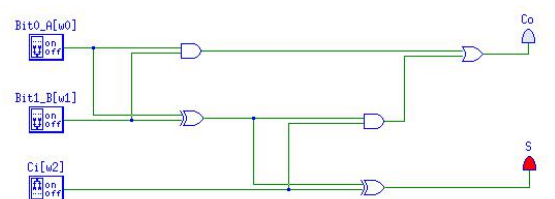
$A = 0 \quad B = 0 \quad C_i = 1 \quad S = 1 \quad C_o = 0$




A = 0 B = 1 Ci = 0 S = 1 Co = 0

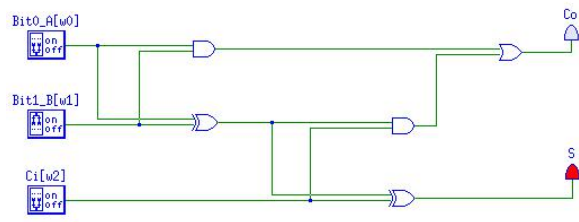


A = 0 B = 1 Ci = 1 S = 0 Co = 1

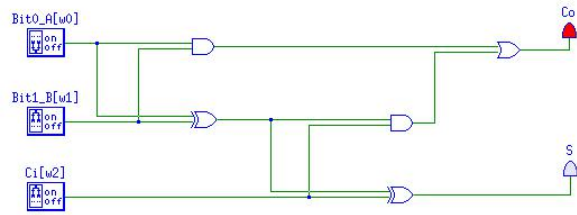


A = 1 B = 0 Ci = 0 S = 1 Co = 0

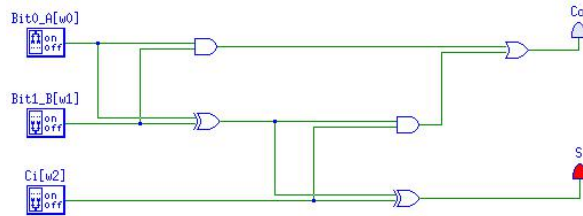

A = 1 B = 0 Ci = 1 S = 0 Co = 1

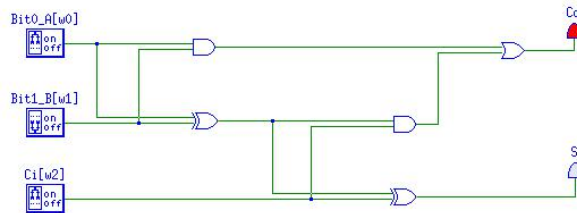

A = 1 B = 1 Ci = 0 S = 0 Co = 1

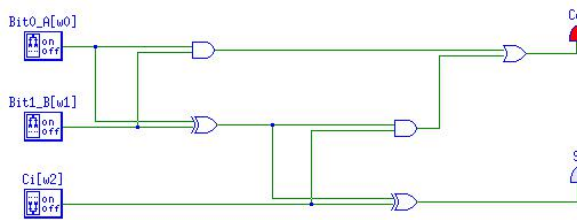

A = 1 B = 1 Ci = 1 S = 1 Co = 1

