 


NAME: MENGYU RAO
 MU ID: 19104294
 FZU ID: 831903230

CS220 Computer Architecture
 Digital Logic Design
 Practical 7

state diagram



state/output table:

	X		Z
	0	1	
1	1	2	0
2	3	2	0
3	4	2	0
4	4	2	1

make secondary state assignment

y_1	y_0	State	Z
0	0	1	0
0	1	2	0
1	0	3	0
1	1	4	1

Transition table

		X			
		0		1	
y_1	y_0	0	0	0	1
0	0	0	0	0	1
0	1	1	0	0	1
1	0	1	1	0	1
1	1	1	1	0	1

excitation table

		X			
		0		1	
y_1	y_0	0	0	0	1
0	0	0	0	0	1
0	1	1	Φ	0	1
1	0	1	1	Φ	1
1	1	1	1	Φ	1
		y_1	y_0	y_1	y_0

excitation equcations:

	00	01	11	10
0	0	I	1	1
1	0	0	Φ	Φ

$$J_1 = \overline{X}y_0 \quad K_1 = X$$

	00	01	11	10
0	0	Φ	1	I
1	I	1	1	I

$$J_0 = X + y_1 \quad K_0 = \overline{X}y_1$$

output eqations:

Z	y_1	y_0
0	0	0
0	0	1
0	1	0
1	1	1

$$Z = y_0 y_1$$


Where y_0 is the output of our first JK Flip Flops and y_1 is the output of our second JK Flip Flops.

Where X is the input of whole circuit.

the circuit:

$$Z = y_0 y_1$$
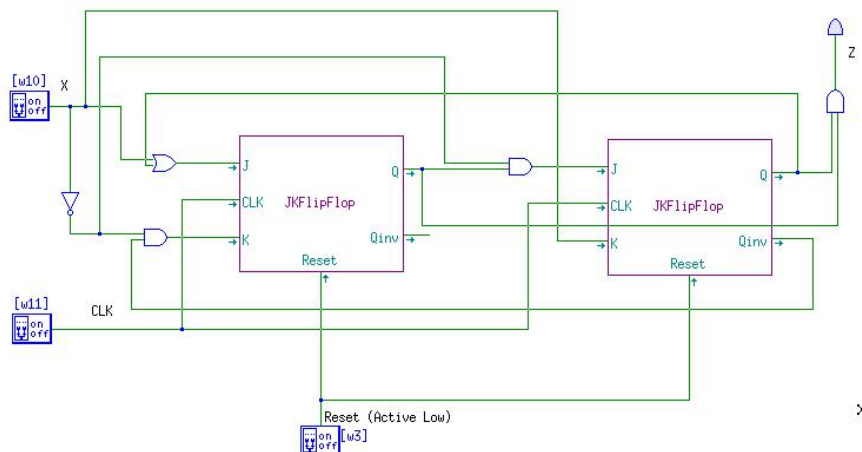
$$J_0 = X + y_1 \quad K_0 = \overline{X}y_1 \quad J_1 = \overline{X}y_0 \quad K_1 = X$$



X is on the left top of the screen.
the JK Flip Flops left is the first Flip Flops.
and the JK Flip Flops right is the second Flip Flops.
Z is on the right top of the screen.
CLK is an switch which is controlled by myself.

the verify of this circuit is recorded by a video

And the circuit works in accordance with the words specification.